

الصفحة الالكترونية لمقررات
الفيزياء لكليات التقنية


المؤسسة العامة للتدريب التقني والمهني
Technical and Vocational Training Corporation



Chapter Six

Kirchhoff's Low

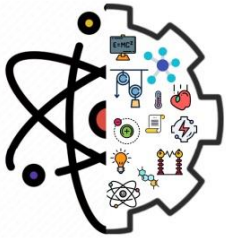Prepared by:
Abdulaziz Alanazi
Abdullah Alsahow




Kirchhoff's laws

That in simple circuits (consisting of straight and parallel connected resistances) current and voltage can be easily found by means of " **Ohm** " law, but in complex circuits it is not possible, so the scientist Kirchhoff developed a law (**Kirchhoff's Laws Circuit**) to analyze complex circuits, namely:-

- 1-the Kirchhoff current law (**KCL**), also known as the law "**conserving Charge**".
- 2-Kirchhoff's law of voltage (**KVL**), also known as the law of "**energy conservation** "

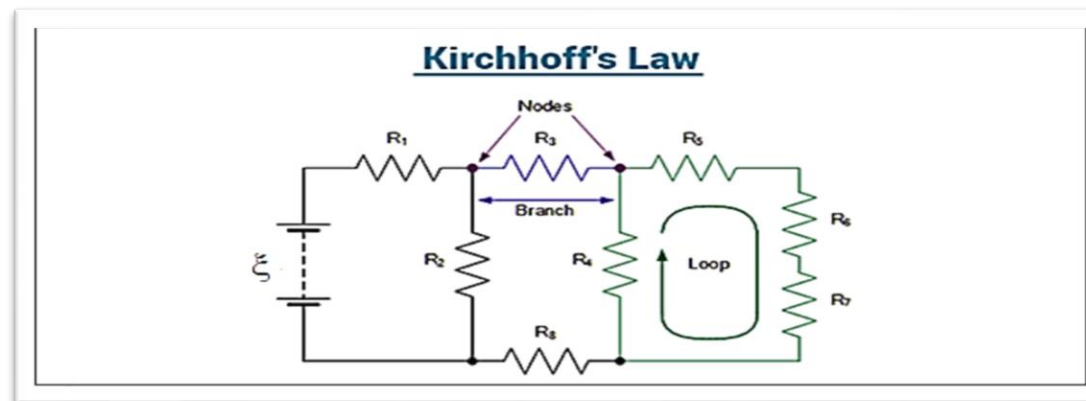The two laws require the definition of the following terms, which are described in the following form:






Important elements:

Node: is a link phrase that connects two or more elements.

Branch: a path that contains one or more elements connecting two nodes.

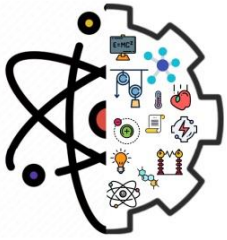Loop: a closed loop in which no element or node is repeated more than once.



Noteworthy

Electric current (I)

An **electric current** is a flow of electric charge in a circuit. and The charge can be negatively charged electrons or positive charge carriers including protons, positive ions.

Electric Voltage (V)


The **Voltage** it is the pressure that forces the charged electrons to flow in an electrical circuit.

Electrical resistance (R)

The **electrical resistance** of an object is a measure of its opposition to the flow of electric current.



The relation between Current and voltage can be given by Ohm's law

$$V = I * R$$

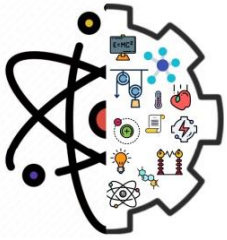



Kirchhoff's Current Law (KCL)

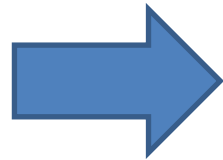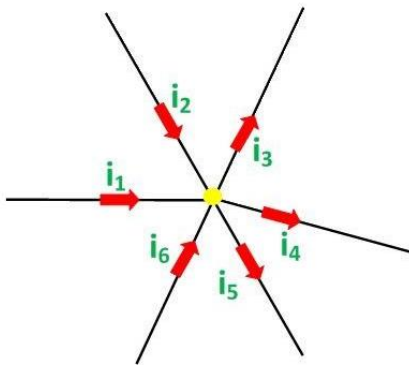Kirchhoff's current law (KCL) states that the sum of currents entering a node is zero.




$$\sum_{n=1}^N i_n = 0$$

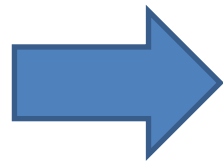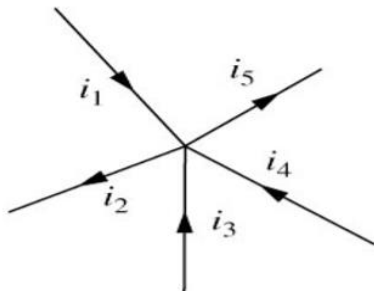Kirchhoff's current law (KCL) states that the total currents entering a node is equal the total currents leaving the node.



$$\sum i_{in} = \sum i_{out}$$
$$i_1 + i_3 + i_4 = i_5 + i_2$$

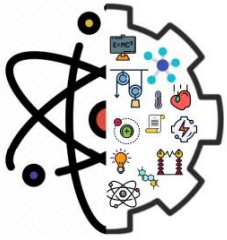

Example 1

From the diagram Find I_3 ?


The Solution


$$I_1 + I_2 = I_3 + I_4$$

Replace each current into its value

$$2 + 9 = I_3 + 4$$

$$I_3 = 2 + 9 - 4 = 7 \text{ A}$$

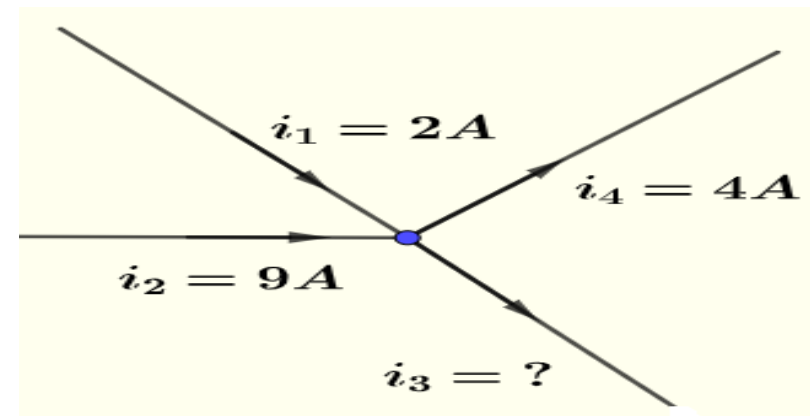

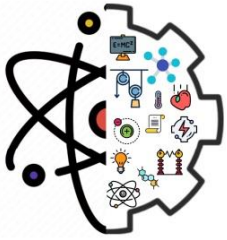

Example 2

For the circuit, use KCL to find the branch currents I_3 and I_4 :


The Solution


That the direction of I_1 and I_3 Inter to the node (n_1):

$$I_1 + I_3 = I_2 \longrightarrow 5 + I_3 = 9 \quad \text{Then : } I_3 = 9 - 5 = 4A$$

That the direction of I_3 and I_4 out to the node (n_2):

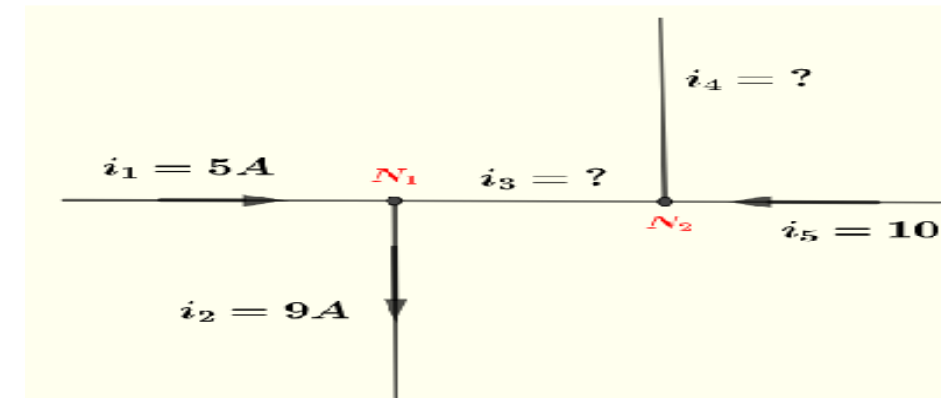
$$I_3 + I_4 = I_5 \longrightarrow 4 + I_4 = 10 \quad \text{Then : } I_4 = 10 - 4 = 6A$$



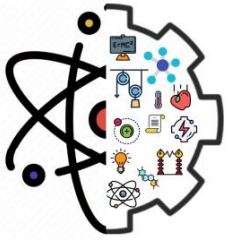


Kirchhoff's Voltage Law (KVL)

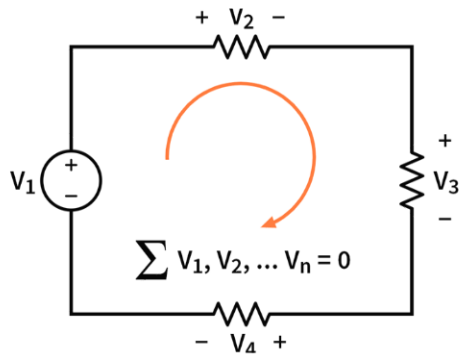Kirchhoff's voltage law (KVL) states that the sum of all voltages around a closed path (or loop) is zero.



Mathematically,

$$\sum_{m=1}^M v_n = 0$$

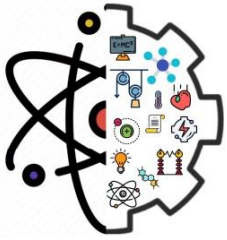

Example 1

For the circuit diagram below, use Kirchhoff's voltage law to find V_A and V_B :

We can start with any branch and go around either clockwise or counterclockwise .

Here we have 2 loops, Suppose we start with the voltage source and go clockwise around the loop as shown:


For Loop 1:

Solution

$$9 - 2 - 1 + V_A = 0 \quad \text{Then : } V_A = -9 + 2 + 1 = -6 \text{ V}$$

For Loop 2:
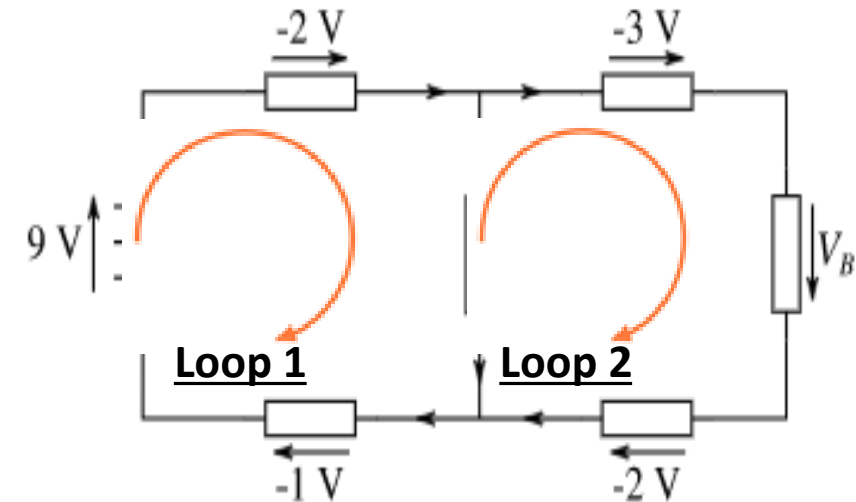
$$V_B - 2 + V_A - 3 = 0 \quad \text{Then : } V_B = -6 + 2 + 3 = -1 \text{ V}$$



الصفحة الالكترونية لمقررات
الفيزياء لكليات التقنية

المؤسسة العامة للتدريب التقني والمهني
Technical and Vocational Training Corporation



Thank you